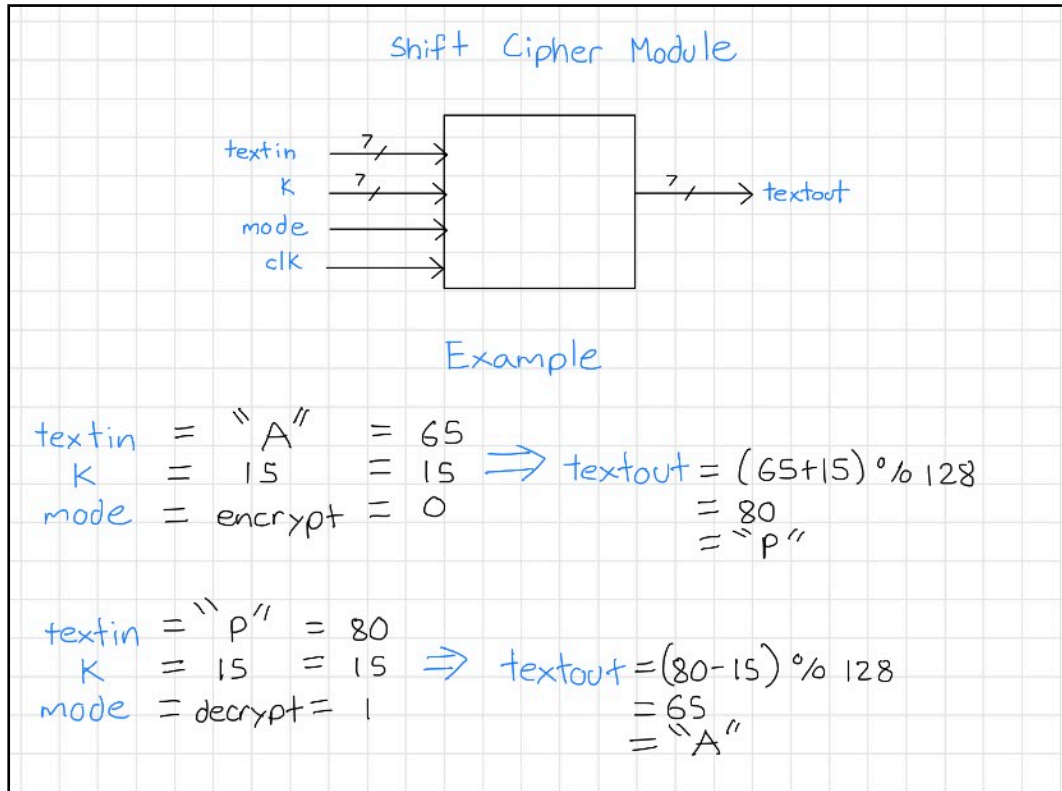


Shift Cipher Using Chisel

Design the sequential circuit shown below using Chisel. The circuit is a shift cipher that encrypts/decrypts one letter at a time. It receives a 7-bit input “textin” and produces a 7-bit output “textout”. These signals represent one of the 128 ASCII characters. This means the key is a 7-bit input. The circuit encrypts if “mode” is zero and decrypts if “mode” is one. Create a test function to test that the circuit works.



```
test(new ShiftCipher) { a =>
  // test encryption
  a.io.textin.poke(65.U)    // "A"
  a.io.key.poke(15.U)
  a.io.mode.poke(0.U)      // encrypt
  a.clock.step(1)
  a.io.textout.expect(80.U) // "P"

  // test decryption
  a.io.textin.poke(80.U)    // "P"
  a.io.key.poke(15.U)
  a.io.mode.poke(1.U)      // decrypt
  a.clock.step(1)
  a.io.textout.expect(65.U) // "A"
}
```

```
println("SUCCESS!!")
```

Elaborating design...

Done elaborating.

test ShiftCipher Success: 0 tests passed in 4 cycles in 0.005329 seconds 750.61 Hz
SUCCESS!!

```
defined class ShiftCipher
```

```

test(new ShiftCipher) { b =>
  for (i <- 0 until 127) {
    for (j <- 0 until 127) {
      // test encryption
      b.io.textin.poke(i.U)
      b.io.key.poke(j.U)
      b.io.mode.poke(0.U)
      b.clock.step(1)
      b.io.textout.expect(((i+j)%128).U)

      // test decryption
      b.io.textin.poke(i.U)
      b.io.key.poke(j.U)
      b.io.mode.poke(1.U)
      b.clock.step(1)
      b.io.textout.expect( (((i-j)%128)+128)%128).U)
    }
  }
}
println("SUCCESS AGAIN!!")

```

Elaborating design...

Done elaborating.

test ShiftCipher Success: 0 tests passed in 4 cycles in 0.004784 seconds 836.11 Hz

SUCCESS!!

Elaborating design...

Done elaborating.

test ShiftCipher Success: 0 tests passed in 32260 cycles in 3.210534 seconds 10048.17 Hz

SUCCESS AGAIN!!

defined class ShiftCipher